

# Lab 6: Performing Rate & Operations


Examples and Deliverables

MAE 405, 2025 Spring


TA: Xinlei Zhang

# To be prepared with OPAMP

- OPAMP (Operational Amplifier)

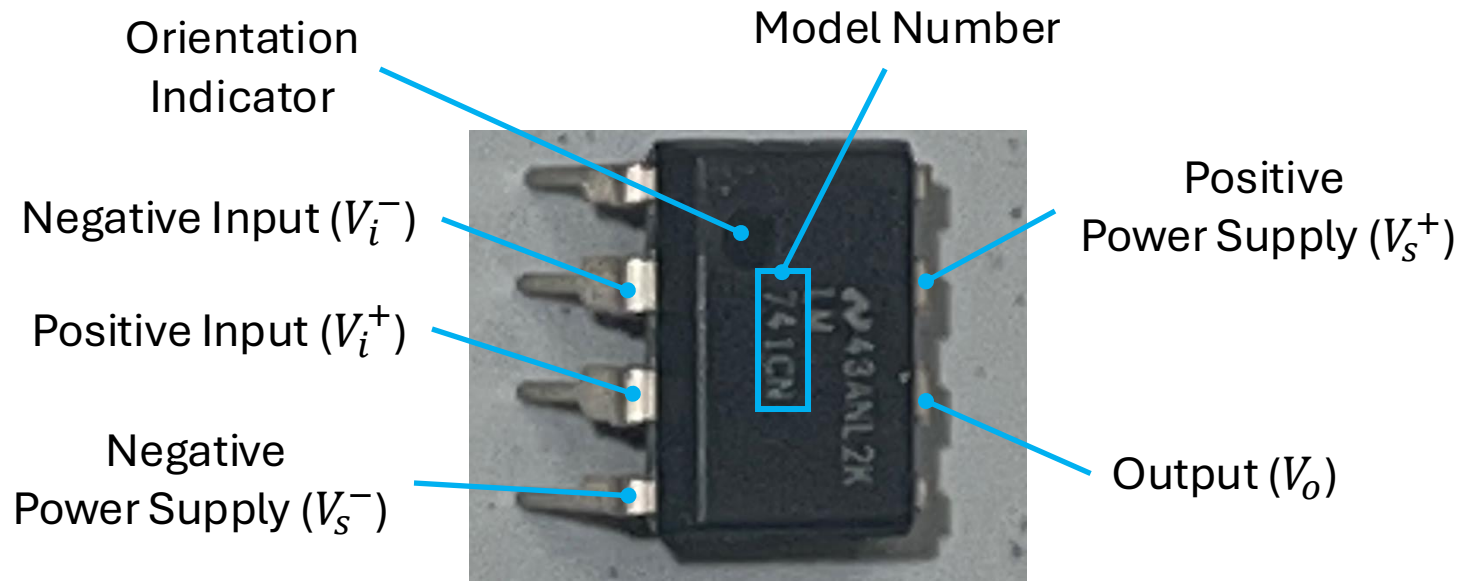

OPAMP 741CN

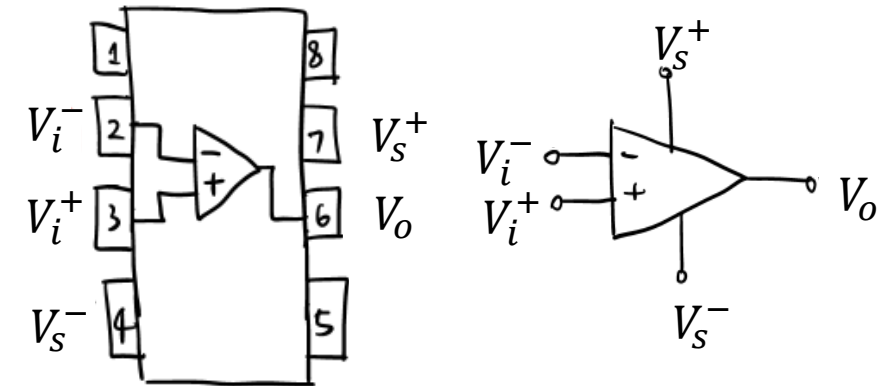


OPAMP Diagram

## Comments:

- Put the Circle (orientation indicator) at the upper-left corner to align the OPAMP with the diagram
- Identify the Model Number – 741CN
- Always power the OPAMP with  $V_s^-$  and  $V_s^+$
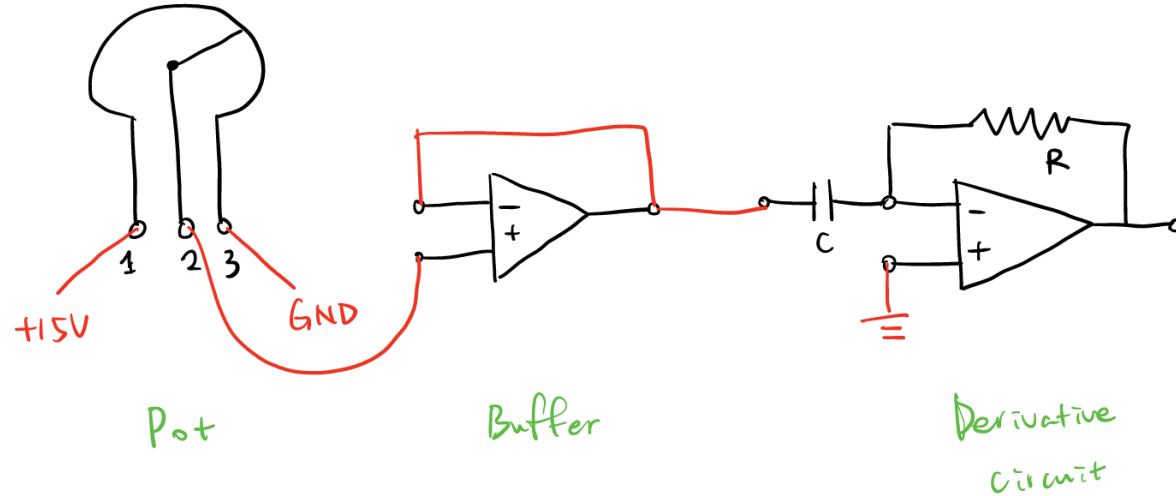
# Circuits will be used



- Connection diagram for the derivative circuit




Buffering (Cascading)

Rate (Derivative)

Area (Integral)

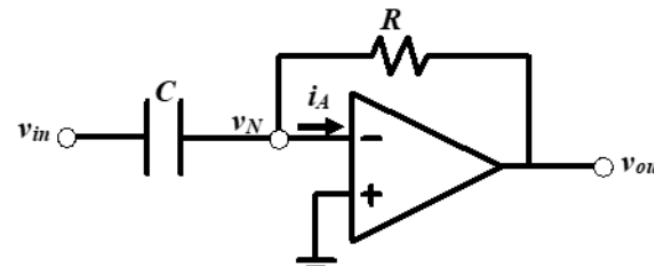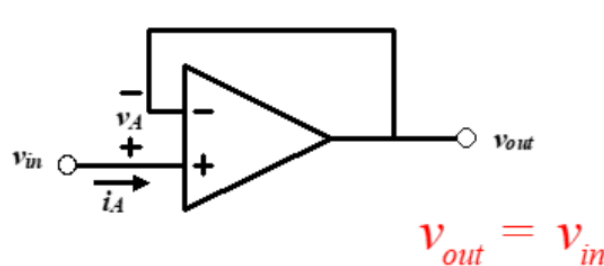
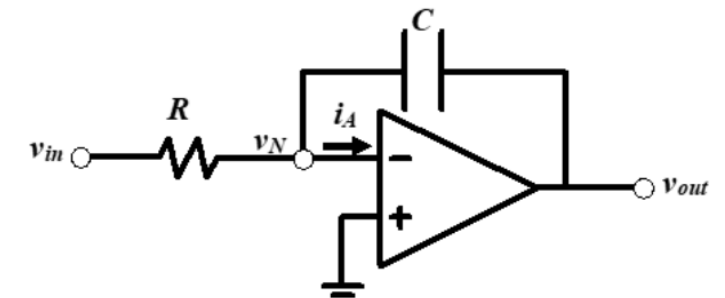
$$v_{out} = -(RC) \text{rate}\{v_{in}\}$$



$$v_{out} = -\left(\frac{1}{RC}\right) \text{area}\{v_{in}\}$$

## Deliverable

- Photo of the Derivative & Integral Circuits

Comment:

- Swap the position of resistor and capacitor to switch between Derivative and Integral Circuit

Suggestion:

- Always compare the diagram and your circuit connection if anything goes wrong